



Ain shams university
Faculty of engineering
Computer engineering and software systems programs

Course: EDA (CSE215)

Project 1

Submitted by: Shehab Ahmed Hassan Kotb

Id: 16p6014

Email: shehabktob@gmail.com

Submitted to: Dr. Mohamed Dessouky
Eng. Michael Hany


2.0 Introduction

This document details the design and implementation of a Digital access control system, this system is designed using MOORE fsm .

The first chapter of this document discusses the design of the system and it's vhdl code, also the testing strategy along with the testing bench code will be provided in this document.

The subsequent chapters will discuss the workflow with alliance tools to reach the final physical layout of the circuit.

3.1 state diagram

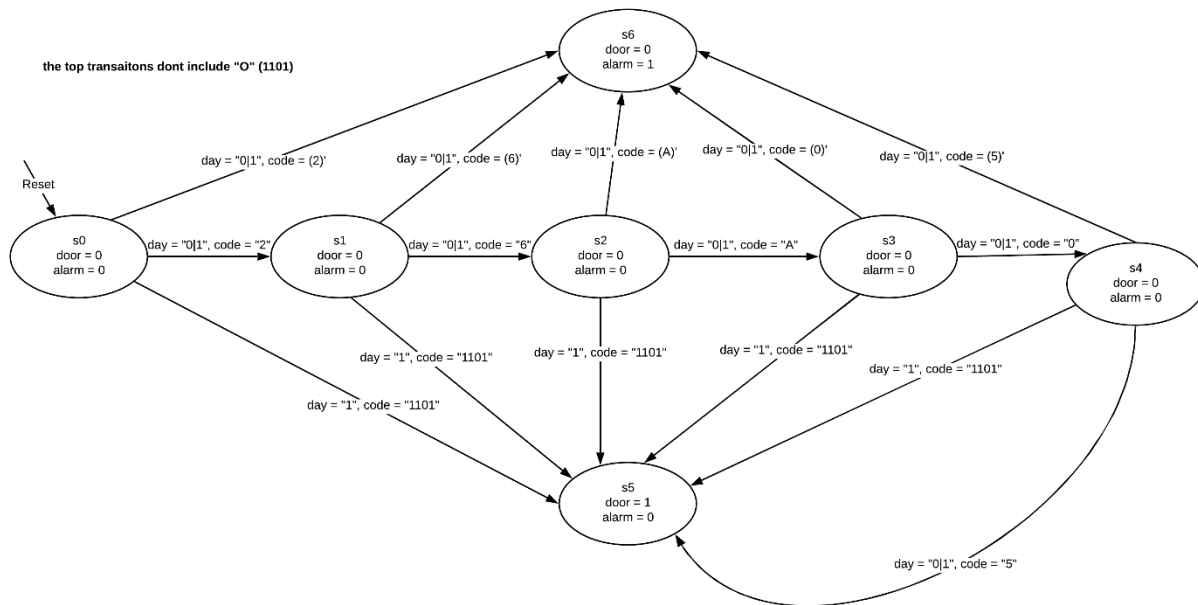

The top transitions don't include code = "O" (1101) which opens the door when is equal to 1.

Moore was chosen over mealy for the following reasons:


- Mealy has combinational paths between inputs and outputs which lead to long paths going through multiple components which slow down the system.
- Since this is an access control system Moore machine may be safer to use, because they change states on the clock edge.
- Moore model has simplified behavior and is easy to design.

3.2 testing bench strategy

tested feature	reset	day	code (hex)	delay	expected (door)	expected (alarm)
normal operation (night)	0	0	2	20 ns	0	0
			6			
			a			
			0			
			5			
reset (night)	1	0	0		1	
					0	0
wrong code (night)	0	0	1		0	1
normal operation (day)	0	1	2		0	0
			6			
			a			
			0			
			5			
reset (day)	1	1	0		1	
					0	0
O button (day)	0	1	1101 (binary)		1	0
wrong code (day)	0	1	1		0	1

We don't cover everything here we just test for basic functionality of the system.

3.3 simulation results

 

```

1  library IEEE;
2  USE ieee.std_logic_1164.ALL;
3
4  entity DigiCode is
5  port (
6      ck      : in  std_logic;
7      vdd     : in  std_logic;
8      vss     : in  std_logic;
9      code    : in  std_logic_vector (3 downto 0);
10     reset   : in  std_logic;
11     day     : in  std_logic;
12     alarm   : out std_logic;
13     door    : out std_logic
14 );
15 end DigiCode;
16
17 architecture MOORE of DigiCode is
18     type STATE_TYPE is (S0, S1, S2, S3, S4, S5, S6);
19     signal NS, CS : STATE_TYPE;
20
21 begin
22     process (CS, reset, code, day)
23     begin
24
25         if (reset='1') then
26             NS<=S0;
27         else
28             case CS is
29                 when S0 =>
30                     if (day='1' and code = "1101") then --code = 0
31                         NS <= S5;
32                     elsif (code = x"2") then
33                         NS <= S1;
34                     else
35                         NS <= S6;
36                     end if;
37
38                 when S1 =>
39                     if (day='1' and code = "1101") then --code = 0
40                         NS <= S5;
41                     elsif (code = x"6") then
42                         NS <= S2;
43                     else
44                         NS <= S6;
45                     end if;
46
47                 when S2 =>
48                     if (day='1' and code = "1101") then --code = 0
49                         NS <= S5;
50                     elsif (code = "1010") then
51                         NS <= S3;
52                     else
53                         NS <= S6;
54                     end if;
55
56                 when S3 =>
57                     if (day='1' and code = "1101") then --code = 0
58                         NS <= S5;
59                     elsif (code = x"0") then
60                         NS <= S4;
61                     else
62                         NS <= S6;
63                     end if;
64
65             end case;
66         end if;

```

```

67
68     when S4 =>
69         if (day='1' and code = "1101") then --code = o
70             NS <= S5;
71         elsif (code = x"5") then
72             NS <= s5;
73         else
74             Ns <= s6;
75         end if;
76
77
78     when S5 =>
79         --door <= '1';
80         null;
81         --alarm <= '0';
82         -- if (day='1' and code == '1101') then --code = o
83             -- NS <= S5;
84         -- elsif (code == '0')
85             -- NS <= s4;
86         -- else
87             -- Ns <= s6;
88         -- end if;
89
90
91     when S6 =>
92         --door <= '0';
93         --alarm <= '1';
94         null;
95         -- if (day='1' and code == '1101') then --code = o
96             -- NS <= S6;
97         -- elsif (code == '0')
98             -- NS <= s5;
99         -- else
100             -- Ns <= s6;
101         -- end if;
102
103     when others => assert(false)
104     report "illegal state" severity error;
105
106
107     end case;
108 end if;
109
110 case cs is
111     when s0 =>
112         door <= '0';
113         alarm <= '0';
114     when s1 =>
115         door <= '0';
116         alarm <= '0';
117     when s2 =>
118         door <= '0';
119         alarm <= '0';
120     when s3 =>
121         door <= '0';
122         alarm <= '0';
123     when s4 =>
124         door <= '0';
125         alarm <= '0';
126     when s5 =>
127         door <= '1';
128         alarm <= '0';
129     when s6 =>
130         door <= '0';
131         alarm <= '1';
132 end case;

```

```
133     end process;
134
135 -- Process (2): State update (sequential)
136 process(ck)
137 begin
138     if(ck = '1' and not ck'stable)then
139         CS <= NS;
140     end if;
141 end process;
142
143 end MOORE;
144
```

Digicode_tb

```
1  library IEEE;
2  USE ieee.std_logic_1164.ALL;
3
4  -- Entity declaration for your testbench. Don't declare any ports here
5  ENTITY testbench_Digicode IS
6  END ENTITY testbench_Digicode;
7
8  ARCHITECTURE test_Digicode OF testbench_Digicode IS
9
10 -- Component Declaration for the Device Under Test (DUT)
11 COMPONENT Digicode IS
12 port (
13     ck      : in  std_logic;
14     vdd     : in  std_logic;
15     vss     : in  std_logic;
16     code    : in  std_logic_vector (3 downto 0);
17     reset   : in  std_logic;
18     day     : in  std_logic;
19     alarm   : out std_logic;
20     door    : out std_logic
21 );
22 END COMPONENT Digicode;
23
24 FOR dut: Digicode USE ENTITY WORK.Digicode (MOORE);
25
26 -- Declare input signals and initialize them
27 SIGNAL ck      : std_logic := '0';
28 SIGNAL vdd     : std_logic := '1';
29 SIGNAL vss     : std_logic := '0';
30 SIGNAL code    : std_logic_vector (3 downto 0) := x"0";
31 SIGNAL alarm   : std_logic := '0';
32 SIGNAL reset   : std_logic := '0';
33 SIGNAL day     : std_logic := '0';
34 SIGNAL door    : std_logic := '0';
35
36 -- Constants and Clock period definitions
37 constant clk_period : time := 20 ns;
38 BEGIN
39
40 -- Instantiate the Device Under Test (DUT)
41 dut: Digicode PORT MAP (ck, vdd, vss, code, reset, day, alarm, door);
42
43 -- Clock process definitions( clock with 50% duty cycle )
44 clk_process :process
45 begin
46     ck <= '0';
47     wait for clk_period/2;
48     ck <= '1';
49     wait for clk_period/2;
50 end process;
51
52 -- Stimulus process, refer to clock signal
53 stim_proc: PROCESS IS
54 BEGIN
55     -- case 1 correct code entered at night "day = 0"
56     code <= x"2";
57     WAIT FOR clk_period;
58     ASSERT alarm = '0' and door = '0'
59     REPORT "output error"
60     SEVERITY error;
61
62     code <= x"6";
63     WAIT FOR clk_period;
64     ASSERT alarm = '0' and door = '0'
65     REPORT "output error"
66     SEVERITY error;
```



```

67
68     code <= x"a";
69     WAIT FOR clk_period;
70     ASSERT alarm = '0' and door = '0'
71     REPORT "output error"
72     SEVERITY error;
73
74     code <= x"0";
75     WAIT FOR clk_period;
76     ASSERT alarm = '0' and door = '0'
77     REPORT "output error"
78     SEVERITY error;
79
80     code <= x"5";
81     WAIT FOR clk_period;
82     ASSERT alarm = '0' and door = '1'
83     REPORT "output error"
84     SEVERITY error;
85
86     --case 2 reset test
87     code <= x"0";
88     reset <= '1';
89     WAIT FOR clk_period;
90     ASSERT alarm = '0' and door = '0'
91     REPORT "output error"
92     SEVERITY error;
93
94     --case 3 testing wrong code at night "day = 0"
95     code <= x"1";
96     reset <= '0';
97     WAIT FOR clk_period;
98     ASSERT alarm = '1' and door = '0'
99     REPORT "output error"
100    SEVERITY error;
101
102    --returning to s0
103    reset <= '1';
104    WAIT FOR clk_period;
105    ASSERT alarm = '0' and door = '0'
106    REPORT "output error"
107    SEVERITY error;
108
109    --case 4 testing correct code with day = 1
110    code <= x"2";
111    day <= '1';
112    reset <= '0';
113    WAIT FOR clk_period;
114    ASSERT alarm = '0' and door = '0'
115    REPORT "output error"
116    SEVERITY error;
117
118    code <= x"6";
119    day <= '1';
120    reset <= '0';
121    WAIT FOR clk_period;
122    ASSERT alarm = '0' and door = '0'
123    REPORT "output error"
124    SEVERITY error;
125
126    code <= x"a";
127    day <= '1';
128    reset <= '0';
129    WAIT FOR clk_period;
130    ASSERT alarm = '0' and door = '0'
131    REPORT "output error"
132    SEVERITY error;

```

```

133
134     code <= x"0";
135     day <= '1';
136     reset <= '0';
137     WAIT FOR clk_period;
138     ASSERT alarm = '0' and door = '0'
139     REPORT "output error"
140     SEVERITY error;
141
142     code <= x"5";
143     day <= '1';
144     reset <= '0';
145     WAIT FOR clk_period;
146     ASSERT alarm = '0' and door = '1'
147     REPORT "output error"
148     SEVERITY error;
149
150     --case 5 testing rest when day = 1
151     reset <= '1';
152     WAIT FOR clk_period;
153     ASSERT alarm = '0' and door = '0'
154     REPORT "output error"
155     SEVERITY error;
156
157     --case 6 testing "o" button when day = 1
158     code <= "1101";
159     day <= '1';
160     reset <= '0';
161     WAIT FOR clk_period;
162     ASSERT alarm = '0' and door = '1'
163     REPORT "output error"
164     SEVERITY error;
165
166     --returning to s0
167     reset <= '1';
168     WAIT FOR clk_period;
169     ASSERT alarm = '0' and door = '0'
170     REPORT "output error"
171     SEVERITY error;
172
173     --case 6 wrong code when day = 1
174     code <= x"1";
175     day <= '1';
176     reset <= '0';
177     WAIT FOR clk_period;
178     ASSERT alarm = '1' and door = '0'
179     REPORT "output error"
180     SEVERITY error;
181
182     --returning to s0
183     reset <= '1';
184     WAIT FOR clk_period;
185     ASSERT alarm = '0' and door = '0'
186     REPORT "output error"
187     SEVERITY error;
188
189
190
191 WAIT; -- stop process simulation run
192
193 END PROCESS stim_proc;
194 END ARCHITECTURE test_DigiCode;
195
196
197

```